

1. (a) $Q^{n+1} = J\bar{Q} + \bar{K}Q$



$Q \rightarrow Q^{n+1}$	J	K
0 0	0	x
0 1	1	x
1 0	x	1
1 1	x	0

(b) $Q^{n+1} = D$


$Q \rightarrow Q^{n+1}$	D
0 0	0
0 1	1
1 0	0
1 1	1

(c) $Q^{n+1} = T \oplus Q$

$Q \rightarrow Q^{n+1}$	T
0 0	0
0 1	1
1 0	1
1 1	0

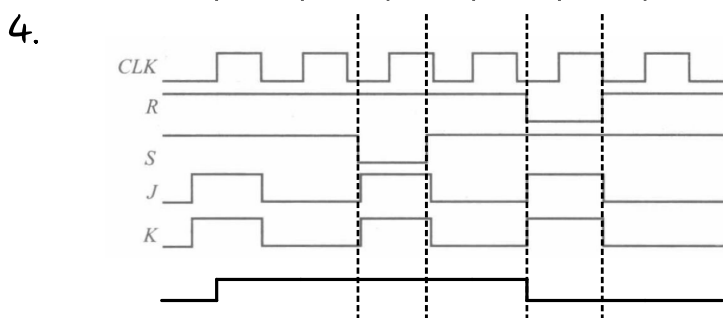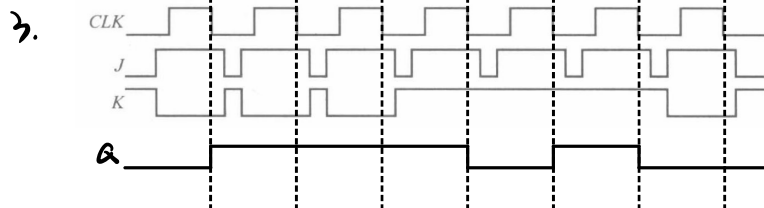


7. $Q = \bar{Q}$ 二分频电路.

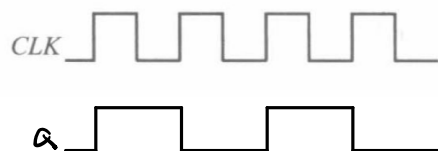

8. (1) $Q^{n+1} = J\bar{Q} + \bar{K}Q$

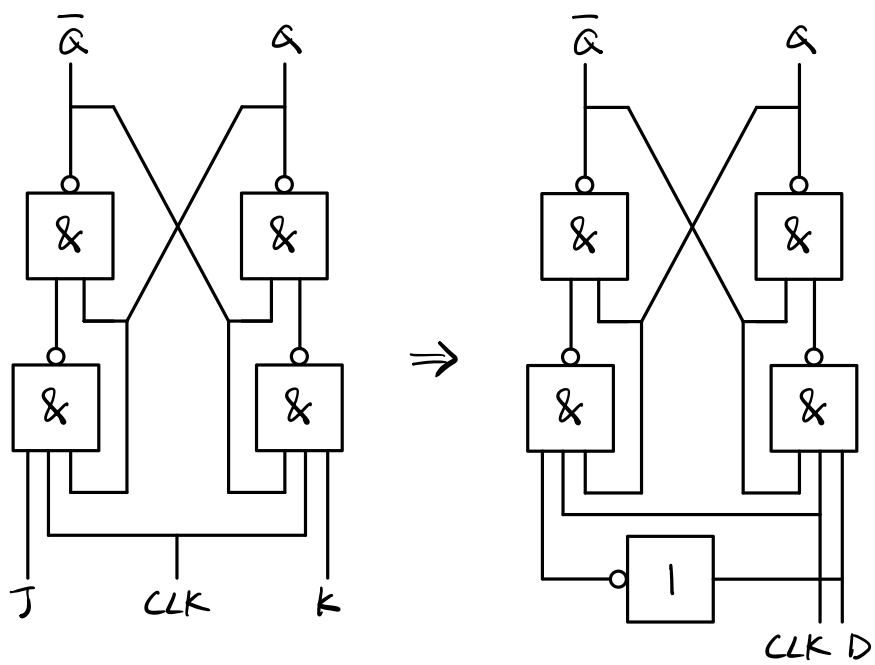(2) $J=D \quad K=\bar{D} \quad Q^{n+1} = D\bar{Q} + \bar{D}Q = D$.



(7)

